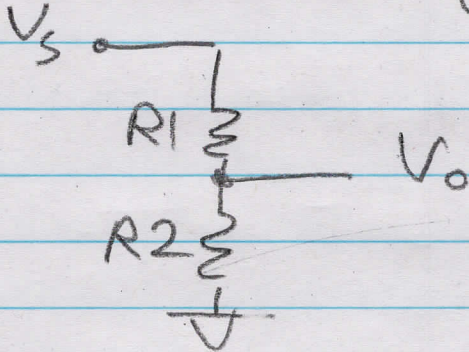


R DIVIDER

- o Circuit and eqns



$$K = \frac{V_o}{V_s} = \frac{R_2}{R_1 + R_2}$$

$$R_{TOT} = R_1 + R_2$$

- o sub $R_1 = R_{TOT} - R_2$ into K

$$K = \frac{R_2}{R_{TOT} - R_2 + R_2} = \frac{R_2}{R_{TOT}}$$

$$R_2 = R_{TOT} \cdot K$$


- o sub $R_2 = R_{TOT} - R_1$ into eqn above

$$\begin{aligned} R_2 &= R_{TOT} \cdot K \\ R_{TOT} - R_1 &= R_{TOT} \cdot K \\ -R_1 &= R_{TOT} \cdot K - R_{TOT} \end{aligned}$$

$$R_1 = R_{TOT} (1 - K)$$

LP FILTER

o Circuit and Eqn

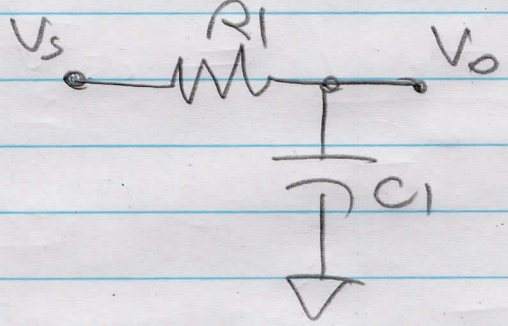

$$H(s) = \frac{1}{1 + \frac{s}{\omega_0}}$$

$$\omega_0 = 2\pi f_c$$

o Magnitude of $H(s)$, Sub $s = 2\pi f j$

$$|H(f)| = \left| \frac{1}{1 + \frac{2\pi f j}{2\pi f_c}} \right|$$

$$= \frac{1}{\sqrt{1 + (f/f_c)^2}}$$

o What is magnitude approx at $f \gg f_c$?

$$|H(f)| = \frac{1}{\sqrt{(f/f_c)^2}} = \frac{f_c}{f}$$

o Cutoff freq ($|H(f)| = -3dB$)

$$\tau = R_1 \cdot C_1$$

$$f_c = \frac{1}{2\pi \tau}$$

$$= \frac{1}{2\pi R_1 \cdot C_1}$$

LP FILTER

o Step Response $V_s = V_s$ is a step input.

$$V_o = V_s (1 - e^{-\frac{t}{\tau}})$$

o Ratio of V_o to V_s

$$\frac{V_o}{V_s} = (1 - e^{-\frac{t}{\tau}})$$

o % Error to final value vs. t

$$\text{Err} = \frac{V_s - V_o}{V_s} = \frac{x\%}{100\%}$$

$$\begin{aligned} &= 1 - \frac{V_o}{V_s} = 1 - (1 - e^{-\frac{t}{\tau}}) \\ &= e^{-\frac{t}{\tau}} \end{aligned}$$

o Solve for time t to % error

$$\ln(\text{Err}) = \frac{-t}{\tau} \cdot \ln(e)$$

$$t = -\frac{\ln(\text{Err}) \cdot \tau}{\ln(e)}$$